


Short Answer & type question

1. Differentiate between loop and nodal analysis.

Node analysis.

- Node analysis uses Kirchhoff's Current Law.
- Node analysis method of finding the potential difference between the element or branch in an electric circuit
- Nodal method needed the number of independent node pair equation is one less than the number of junction in the network. That is if n denotes the number of junction in the network and j is the number of independent node equation


Circuit diagram of Nodal analysis

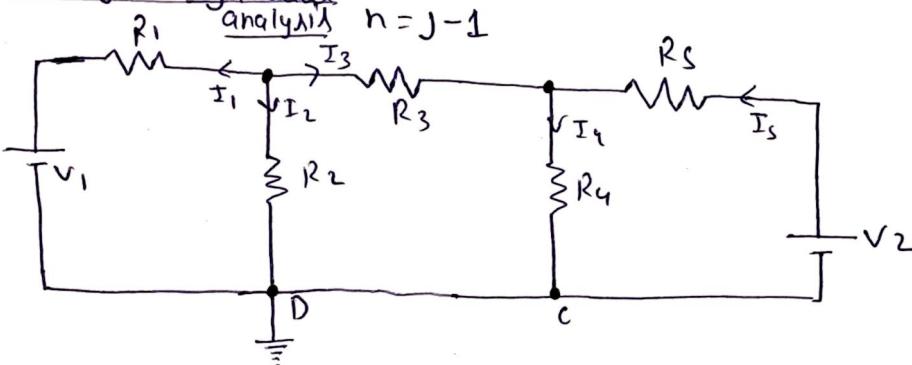

loop analysis.

- Loop analysis use Kirchhoff's Voltage Law.
- In loop analysis method a distinct current is assumed in the loop and the polarities of drops in each element in the loop are determined by the assumed direction of loop current for that loop.
- In loop analysis in any closed circuit the net voltage applied is equal to the sum of the product of current and resistance or in another word in any closed circuit the sum of the voltage rise is equal to the sum of voltage drop in the direction of current flow.

Circuit diagram of loop analysis.

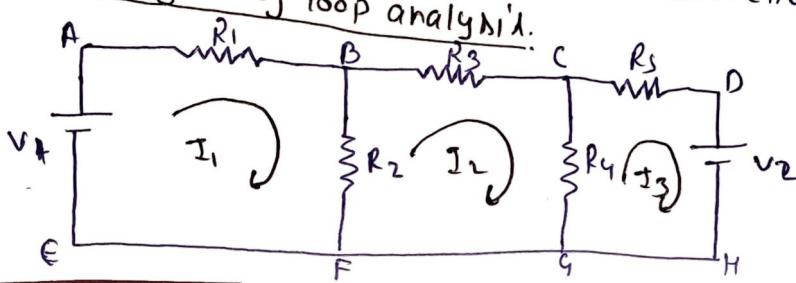


2. Classify source transformation.

Source transformation simply mean replacing one source by an equivalent source. A practical voltage source can be transformed into an equivalent practical current source and similarly a practical current source into voltage source.

Type of Source transformation.


1. Voltage source into current source.

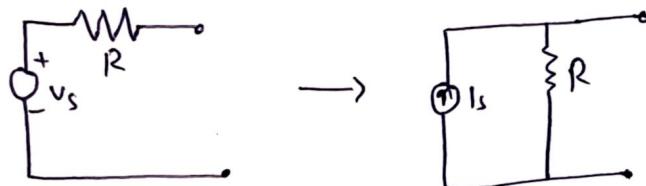

When the voltage source is connected with the resistance in series and it has to be converted into the current source then the resistance is connected in parallel with the current source as shown in the above figure.

$$I_s = V_s / R$$

2. Current source into voltage source.

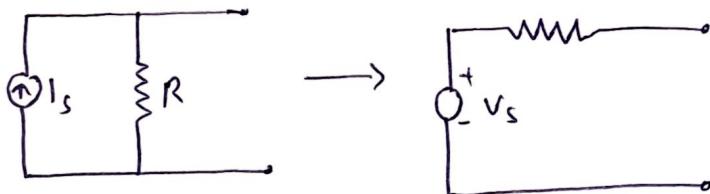

In the above circuit diagram a ~~current~~ current source which is connected in parallel with the resistance is transformed into voltage source by placing the resistance in series with the voltage source.

$$V_s = I_s / R$$

3. Illustrate necessity and advantages of three-phase system.

A three-phase system is a widely used electrical power system that consists of three alternating currents of the same frequency with each phase separated by 120° .

Necessity of three-phase system.

Increased power transmission efficiency.



Power transmission and distribution is cheaper & reliable. & more versatile in case of three-phase system.

Balanced load.

This is essential for high demand industrial and grid requiring stable and efficient energy distribution.

Advantages of three-phase system.

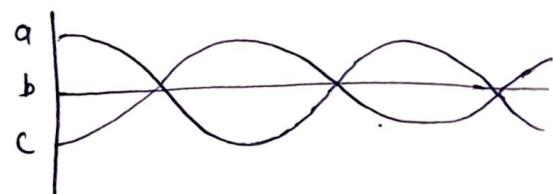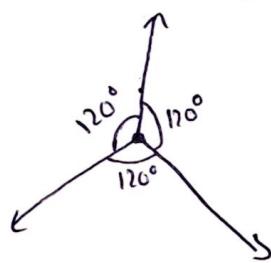- In single phase circuit phase a pulsating power in a three phase circuit the power is constant.
- Output of a three phase machine is more than single phase machine for given volume & weight.
- Three phase machine are smaller than single phase machine for given output.
- The phase machine have higher efficiency and power factor.



4. Classify power losses in transformer.

Losses in transformer.

Total power losses originating in a xmer under loaded condition can be classified into the following group.

Iron losses

Caused by varying magnetization and occur in xmer loss. Iron losses can be further classified as "Hysteresis loss" and "Eddy loss" copper losses.

Caused by the flow of current and occur in primary and secondary winding.

Hysteresis loss.

Occurring in the magnetic frame of the xmer depend upon the following.

(i) Volume of the core

(ii) Frequency of magnetic flux.

Eddy current loss.

It due to the flow of eddy current in the magnetic core and yoke of the xmer, caused by small emf induced in the magnetic frame.

(i) Frequency of flux (f)

(ii) Volume of core.

(iii) maximum value of flux density in core. (B_{max}).

In general copper losses in all these part of the xmer that carry electric current. Copper losses are directly proportional to.

(i) the square of current


(ii) Resistance.

Thus, cu. occurring in the secondary winding = $I^2 p R_p$,

Cu losses occurring in the secondary winding = $I_s^2 R_s$.

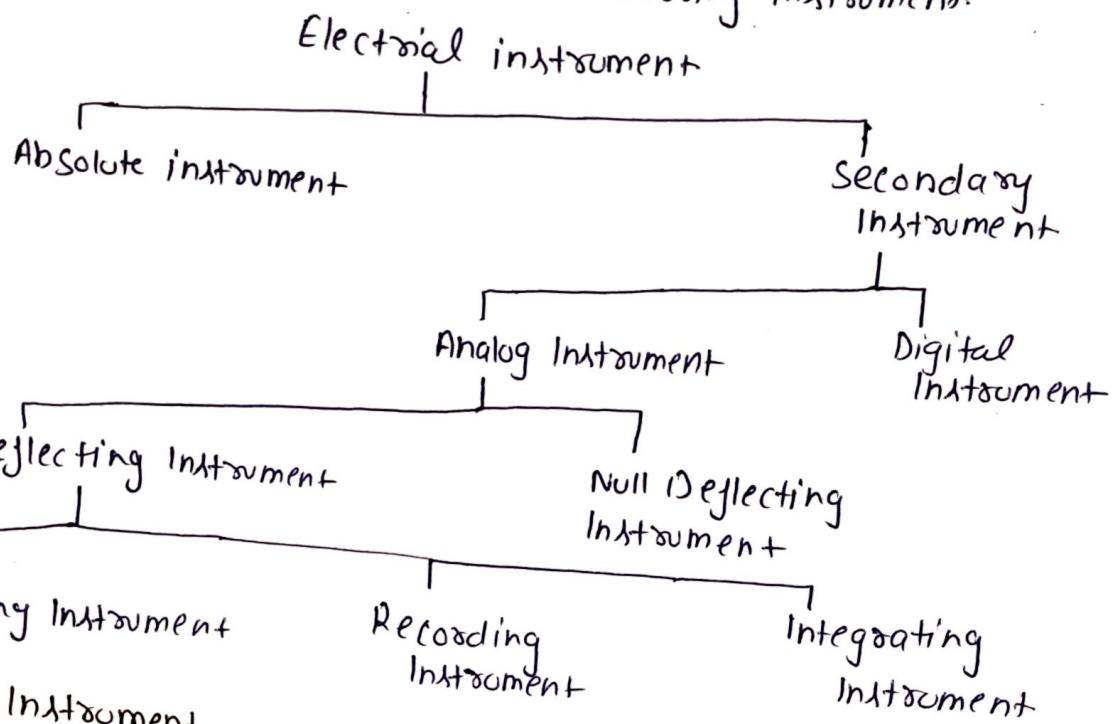5. Classify different type of measuring instrument.

Devices which are used to measure the electrical current, voltage, resistance and power are known as measuring instrument.



Absolute Instrument

This instrument give the value of the electrical quantity to galvanometer.

A galvanometer is an electromechanical measuring instrument for electric current measure the flow of current Ammeter.

A ammeter is an instrument used to measured the current in a circuit.

Voltmeter

A Voltmeter is an instrument used for measuring electric potential difference b/w two point wattmeter.

The wattmeter is an instrument for measuring the electric active power in watt of any given circuit.


6. Describe auto-transformer.

An auto-transformer with only one winding wound on a laminated core. An auto transformer is similar to a two winding transformer but differ in the way the primary and secondary winding are interrelated. A part of the winding is common to both primary and secondary side.

On load condition, a part of the load current is obtained directly from the supply and the remaining part is obtained by transformer action.

In an ordinary transformer, the primary and the secondary winding are electrically insulated from each other but connected magnetically as shown in the figure below. While in auto transformer the primary and the secondary winding are connected magnetically as well as electrically. In fact a part of the single continuous winding is common to both primary and secondary.


There are two types of auto transformer based on the construction. In one type of transformer, there is a continuous winding with the taps brought out at convenient points determined by the desired secondary voltage. In another type of auto transformer there are two or more distinct coils which are electrically connected to form a continuous winding. The construction of auto transformer is shown in the figure below.

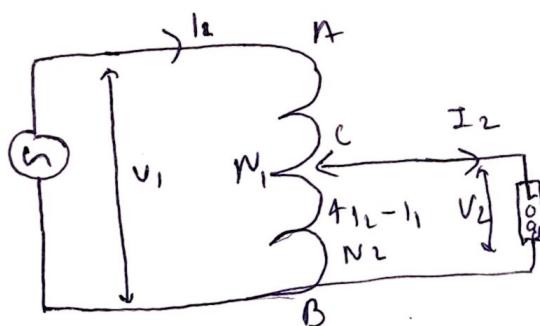

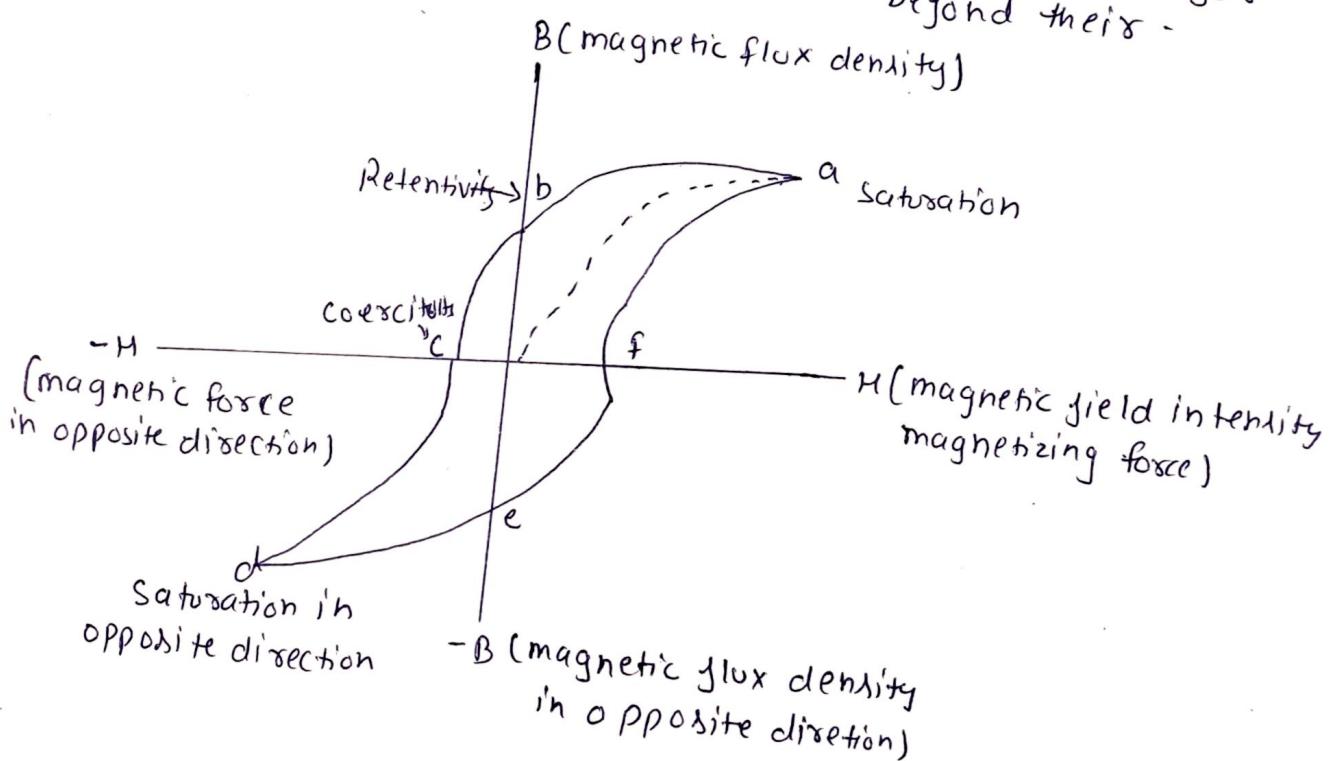7. DIACUM B-H CURVE


The hysteresis loop is a key feature of the BH curve of magnetic material. It represent the energy lost the occur when the magnetic material undergoes a complete cycle of magnetization and demagnetization. The loop highlight the phenomenon where the magnetization lag behind the applied magnetic field. The hysteresis loop is vital in understanding the energy loss in magnetic material used in transformer inductor and electrical motor. A large loop indicate greater energy loss, while a smaller loop indicate lower energy loss. It offer a clear understanding of a material magnetic properties, helping in the characterization of ferromagnetic material.

The area inside the hysteresis loop help in determined energy loss which is crucial for designing energy efficient devices. Help in saturation point identification by analysing the curve ensuring that material do not operate beyond their magnetic capacity.



(Q) Explain R-L-C series circuit.

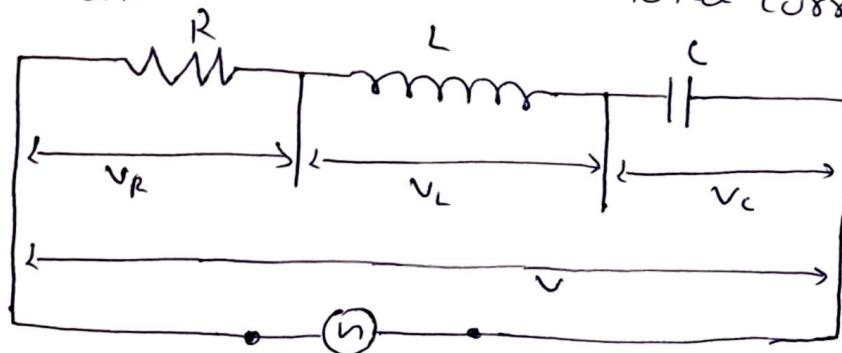When a pure resistance of R ohm, a pure inductance of L Henry and a pure capacitor of C farads are connected together in series combination with each other then RLC Series circuit is formed. As all the three elements are connected in series so, the current flowing through each element of the circuit will be the same as the total current I flowing in the circuit.



$$X_L = 2\pi f L \quad \text{and} \quad X_C = 1/(2\pi f C)$$

Working

When the AC voltage is applied through RLC Series circuit the resulting current I flows through the circuit and thus the voltage across each element will be

$V_R = IR$ that is the voltage across the resistance R and it is in phase with the current I .

$V_L = IX_L$ that is the voltage across the inductance L and it leads the current I by an angle of 90° .

$V_C = IX_C$ that is the voltage across capacitor C and it lags the current by an angle of 90° .


9. Explain pure resistive circuit.

The circuit containing only pure resistance of R ohms in the AC circuit is known as pure resistive AC circuit. The presence of inductance and capacitance does not exist in a purely resistive circuit. The alternating current and voltage both move forward as well as backwards in both the direction of the circuit. The alternating current and voltage follow a shape of the sine wave or known as the sinusoidal waveform.

In the purely resistive circuit, the power is dissipate by the resistor and the phase of the voltage and current remain same both the voltage and current reach their maximum value at the same time. The resistor is the passive device which neither produce nor consume electric power.

In an AC circuit, the ratio of voltage to current depend upon the supply frequency Phase angle and phase difference.

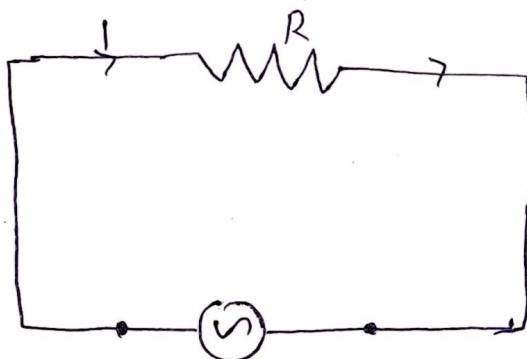In an AC resistive circuit the value of resistance of the resistor will be same irrespective of the supply frequency.




$$V = V_m \sin \omega t$$

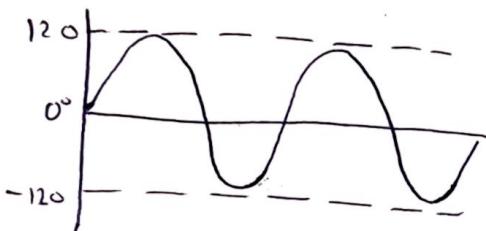10. Compare Single-phase ac System and three-phase ac System.

Single-phase.


- The Single phase requires two wire for completing the circuit the conductor and the neutral the conductor carries the current and the neutral. The conductor carries the current.



- The single phase carry 230°V
- The single phase has the minimum power transfer capability.
- The single phase has simple network
- The single phase has maximum LOM
- The single phase is used for home appliances

three-phase.

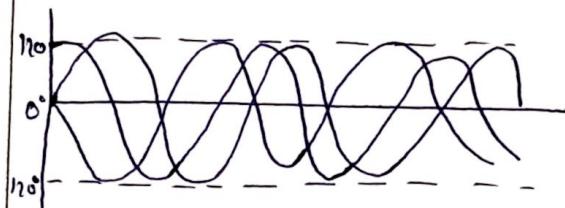
- Three-phase System consist four wire, three conductors and one neutral. The conductors are out of phase and space 120° apart from each other the three phase system.



- The three phase carry 415V
- The three phase have maximum power transfer capability.
- The three phase has complicated network.
- The three phase has minimum LOM
- The three phase is used in large industries and for running heavy load.

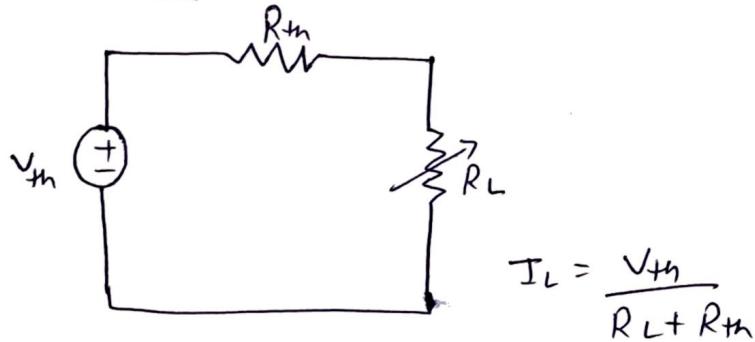11. Explain maximum power transfer theorem

It states that the equivalent source will transfer the maximum power to load resistance if the value of load resistance is equal to the Thevenin's equivalent resistance.



According to maximum power transfer theorem the source V_{th} will transfer to load if $R_L = R_{th}$

Proof.

$$I_L = \frac{V_{th}}{R_{th} + R_L} \quad P_L = I_L^2 R_L$$

$$P_L = \left(\frac{V_{th}}{R_{th} + R_L} \right)^2 \cdot R_L$$

for maximum power transfer $\frac{dP_L}{dR_L} = 0$

$$\frac{dP_L}{dR_L} = \frac{d}{dR_L} \left[\left(\frac{V_{th}}{R_{th} + R_L} \right)^2 \cdot R_L \right] = 0$$

$$\frac{d}{dR_L} \frac{V_{th}^2 \cdot R_L}{(R_{th} + R_L)^2} = 0$$

$$\frac{1}{(R_{th} + R_L)^2} \cdot \left[(R_{th} + R_L)^2 \frac{d}{dR_L} (V_{th}^2 \cdot R_L) - V_{th}^2 R_L \frac{d}{dR_L} (R_{th} + R_L)^2 \right] = 0$$

$$\frac{1}{(R_{th} + R_L)^4} \left[(R_{th} + R_L)^2 \cdot V_{th}^2 - V_{th}^2 R_L \cdot 2(R_{th} + R_L) \right] = 0$$

$$\frac{R_{th} + R_L}{(R_{th} + R_L)^4} \left[(R_{th} + R_L)^2 V_{th} - V_{th}^2 R_L \cdot 2 \right] = 0$$

$$\frac{V_{th}^2}{(R_{th} + R_L)^3} \left[R_{th} + R_L - 2 R_L \right] = 0$$

$$R_{th} + R_L - 2 R_L = 0$$

$$R_{th} + R_L = 2 R_L$$

$$\boxed{R_{th} = R_L}$$


12. Illustrate Thevenin's theorem.

It states that in any linear active bilateral network across its load terminals can be replaced by single voltage source and one series resistance

Principle

Procedure

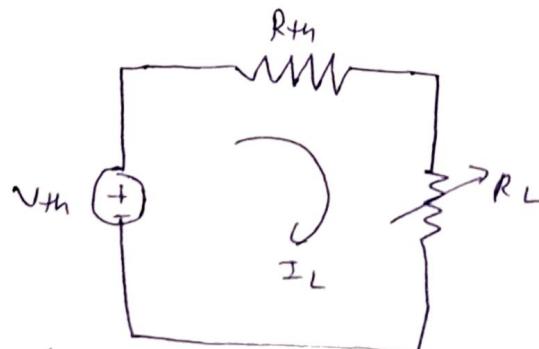- I. first of all remove that load resistance if any.
- II. Now determine the open circuit voltage across the load terminal by using Maxwell loop (or) node method this is V_{th} = Thevenin's Voltage.
- III. Replace all independent source by their internal resistance now find the equivalent resistance add the load terminal R_{th}
- IV. Now draw thevenin's equivalent circuit than connect the load resistance if any



I_L = load current


V_{th} = Thevenin voltage

R_{th} = Thevenin resistance

$$I_L = \frac{V_{th}}{R_{th} + R_L}$$

Long Answer type question

1. Derive emf equation of transformer.

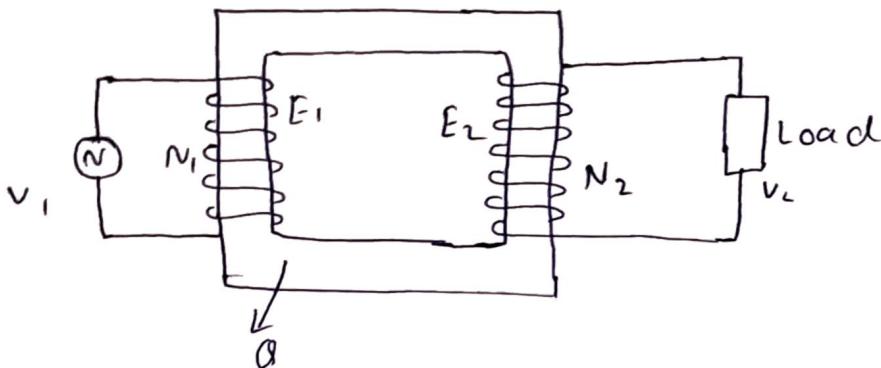

Let us consider that N_1 & N_2 are the no of turns in the Primary & Secondary respectively of a transformer
let the primary winding is excited by a voltage V .

Primary winding suppose f_B is the frequency of supplied voltage.

Due to ~~del~~ alternating current I_1 , there is an alternating NMF $N_1 I_1$, as a result an alternating flux.
The instantaneous flux is given by

$$\phi = \phi_m \sin \omega t$$

$$\phi = \phi_m \sin 2\pi f t$$

where ϕ_m is the maximum value of flux in the core

- A self induced Emf in primary winding.

- A mutually induced Emf in the secondary winding.

$$\begin{aligned}
 e_1 &= -\frac{N_1 d\phi}{dt} \\
 &= -N_1 \frac{d}{dt} (\phi_m \sin 2\pi ft) \\
 &= -N_1 \phi_m 2\pi f \cos 2\pi ft \\
 &= -N_1 \phi_m 2\pi f \sin(2\pi ft - \pi/2) \\
 &= N_1 \phi_m 2\pi f \sin\left(\frac{\pi}{2} - 2\pi ft\right)
 \end{aligned}$$

thus we see that the emf induced in the coil, let the flux induced by an angle of 90°

$$E_{max} = \omega \phi_m N_1$$

$$E_{max} = N_1 \phi_m 2\pi f$$

$$E_{rms} = \frac{E_{max}}{\sqrt{2}} = E_1 = \frac{2\pi f}{\sqrt{2}} N_1 \phi_m$$

$$E_1 = \sqrt{2} \pi f N_1 \phi_m$$

$$E_2 = \sqrt{2} \pi f N_2 \phi_m$$

$$\phi = \phi_m \sin \omega t = \phi_m \sin 2\pi ft$$

$$e_1 = -N_1 \frac{d\phi}{dt}$$


2. Explain resonance of R-L-C series circuit.

Resonance in AC circuit implies a special frequency determined by the value of the resistance, capacitance and inductance for series resonance is straightforward and it is characterized by minimum impedance and zero phase parallel resonance which is more common in electronic practice, requires a more careful definition.

minimum impedance at resonant frequency.


$$I = \frac{V}{Z}$$

$$\omega_0 = \frac{1}{\sqrt{LC}}$$

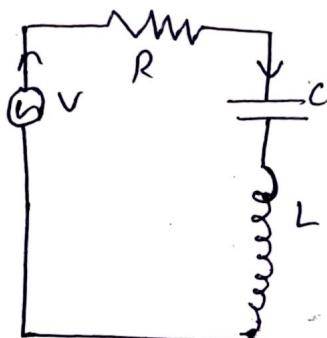

Series resonance.

minimum impedance at resonant frequency.

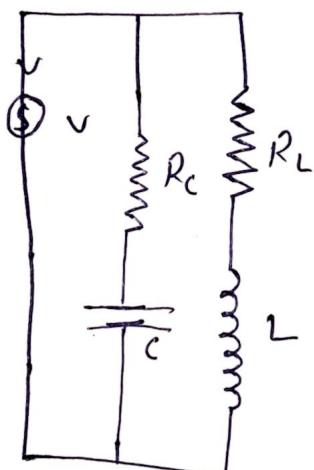

$$\omega_0 \approx \frac{1}{\sqrt{LC}}$$

$$I = \frac{V}{Z}$$

Parallel resonance